

Spectral Graph Theory – Electric Flow

Zhiwei Zhang

March 15, 2019

1 Introduction

In this notes, we are going to discuss the interesting properties when turning a graph into a network of resistors.

1.1 Electrical Laws

First recall some E&M Laws:

$$\begin{array}{ll} I = \frac{U}{R} & \text{Ohm's law} \\ E = I^2 R & \text{Energy formula} \\ |I_{v,in}| = |I_{v,out}| & \text{conservation of flow} \end{array}$$

Note that the last law only holds for nodes that are not source or sink.

1.2 Formation on Graph

We will write a matrix formation of the problem.

- Let $G(V, E)$ be an undirected graph with $|V| = n, |E| = m$.
- Let $v \in \mathbb{R}^n$ be the vector representing the potentials of vertices.
- Edges represent the resistors, and $\forall e(u, v) \in E$. Edge e has resistance r_e .
- Let $f \in \mathbb{R}^m$ representing the flow of all edges, where $f(a, b)$ represents the flow from a to b with. Since $f(a, b)$ is directed, we have $f(a, b) = -f(b, a)$.
- Let weight $w_e = \frac{1}{r_e}$, or the "conductance" of e .

2 Matrix Formation

We also define $f_{ext}(a) = \sum_{b:(a,b) \in E} f(a,b)$, and $f_{ext}(a)$ basically denotes the external current on a , which is **positive number if a is source, negative number with equal magnitude if a is sink, and zero otherwise**. So f_{ext} is a very sparse vector.

Ohm's law directly states that $f(a,b) = \frac{v(a)-v(b)}{r_{a,b}} = w_{a,b}(v(a) - v(b))$, therefore

$$\sum_{b:(a,b) \in E} f(a,b) = \sum_{b:(a,b) \in E} w_{a,b}(v(a) - v(b)) = d(a)v(a) - \sum_{b:(a,b) \in E} w_{a,b}v(b)$$

where $d(a) = \sum_{b:(a,b) \in E} w_{a,b}$, the weighted degree of a .

Notice that $d(a), w_{a,b}$ are entries of the weighted laplacian L_G , and through simple verification, we can show that the equation above is equivalent to $L_G v = f_{ext}$